



# Embracing the quantum future: fundamental training for UPT students

Multiple qubits and quantum circuits

Mihai Udrescu (UPT)

$\Rightarrow$  Do NAND

$\Rightarrow$  Do NOR

# Universal Quantum Gates

- Deutsch

Universal gate

$n$ -qubit state  
 $2^n$ -elements

$$D(\theta): |x, y, z\rangle \Rightarrow \begin{cases} i \cos\theta |x, y, z\rangle + \sin\theta |x, y, 1-z\rangle & x = y = 1 \\ |x, y, z\rangle & \text{otherwise} \end{cases}$$


- \* Di Vincenzo

$2^n \times 2^n$  matrix

$$U_2(\omega, \alpha, \beta, \phi) = e^{-i\phi} \begin{bmatrix} e^{i\alpha} \cos\omega & -e^{-i\phi} \sin\omega \\ e^{i\phi} \sin\omega & e^{-i\alpha} \cos\omega \end{bmatrix}$$

$$XOR = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

Universal gate set

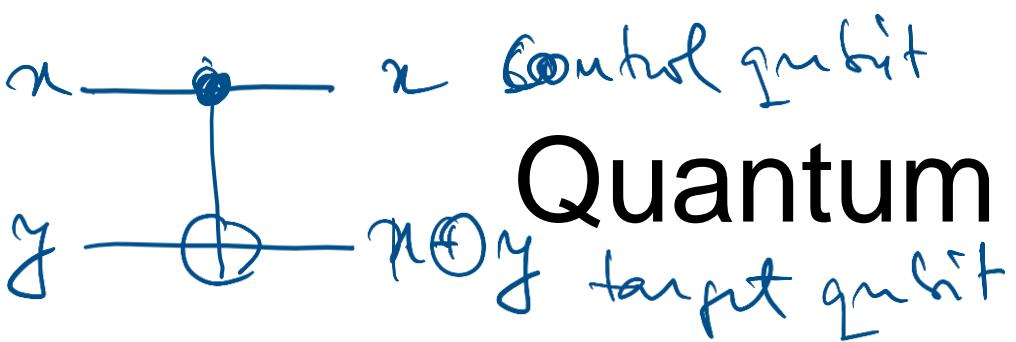

# Quantum Gates

John Preskill

- Pseudo-classical operators


$$PC|\psi\rangle = PC \sum_{i=0}^{2^n-1} a_i |i\rangle = \sum_{i=0}^{2^n-1} a_i |p(i)\rangle$$

$p(k)$  is a permutation over the eigenvectors

- XOR :  $|x, y\rangle \rightarrow |x, x \oplus y\rangle$

$$\begin{aligned}
 00 &\rightarrow 00 \\
 01 &\rightarrow 01 \\
 10 &\rightarrow 11 \\
 11 &\rightarrow 10
 \end{aligned}$$

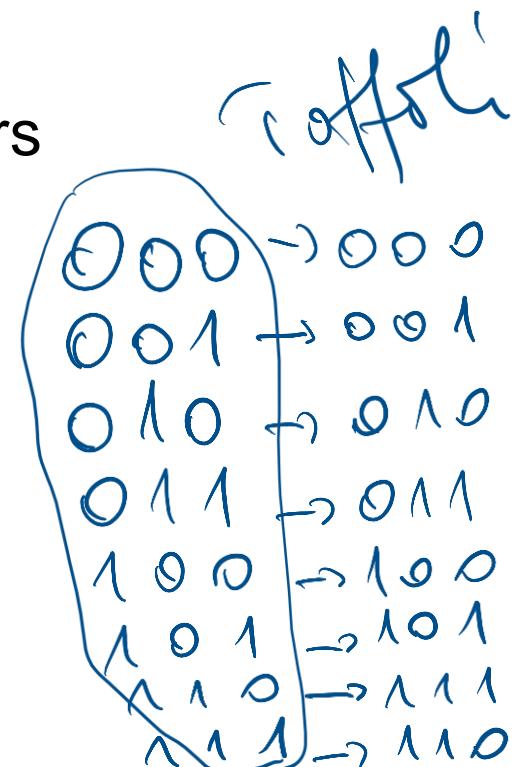
$$XOR = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$



# Quantum Gates

- Toffoli Gate:

$$TOFF: |x, y, z\rangle \rightarrow |x, y, (x \cdot y) \oplus z\rangle$$

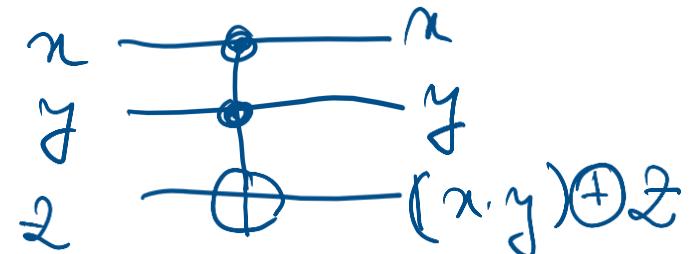

$$TOFF|\psi\rangle = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} a_0 \\ a_1 \\ a_2 \\ a_3 \\ a_4 \\ a_5 \\ a_6 \\ a_7 \end{bmatrix} = \begin{bmatrix} a_0 \\ a_1 \\ a_2 \\ a_3 \\ a_4 \\ a_5 \\ a_7 \\ a_6 \end{bmatrix}$$

Handwritten annotations above the matrix show the input state  $|0000000\rangle$  and the output state  $|110111\rangle$ . Handwritten annotations to the right of the matrix show the final state  $|a_0 a_1 a_2 a_3 a_4 a_5 a_6 a_7\rangle$  with values  $000$ ,  $001$ ,  $a_2$ ,  $a_3$ ,  $a_4$ ,  $a_5$ ,  $110$ , and  $111$  respectively.

# Useful Unitary Gates

- Hadamard gate

$$H = \begin{bmatrix} \frac{1}{\sqrt{2}} & \frac{1}{\sqrt{2}} \\ \frac{1}{\sqrt{2}} & -\frac{1}{\sqrt{2}} \end{bmatrix} = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix}$$

$$\begin{aligned} |\Psi\rangle &= H \otimes H \otimes \dots \otimes H |00\dots 0\rangle = H^{\otimes n} |0\rangle^{\otimes n} \\ &= \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \otimes \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \otimes \dots \otimes \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \\ &= \frac{1}{2^n} (|00\dots 0\rangle + |00\dots 0\rangle + \dots + |11\dots 1\rangle) \\ &= \frac{1}{2^n} \sum_{i=0}^{2^n-1} |i\rangle \end{aligned}$$

$$\left\{ \begin{array}{l}
 |\psi\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \\
 |\psi\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \\
 \vdots \\
 |\psi\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle)
 \end{array} \right. = \underbrace{\left[ \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \right]^{\otimes n}}_{\text{H}^{\otimes n} \text{ on } |\psi\rangle} \quad \left. \begin{array}{l}
 |\psi\rangle = \frac{1}{\sqrt{2}} \sum_{i=1}^{2^n-1} |i\rangle
 \end{array} \right\}$$

id Quantique

$$H^{\otimes 2} \rightarrow \boxed{H} + \boxed{H}$$

$$H \cdot H \rightarrow \boxed{H} - \boxed{H} - \cancel{H}$$

(II)

$$\begin{aligned}
 H \cdot H &= \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix} \cdot \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 2 & 0 \\ 0 & 2 \end{pmatrix} \\
 &= \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} = I
 \end{aligned}$$

# Useful Unitary Gates

- Qubit rotation

around axis  $y$

$$R_y(\theta) = \begin{bmatrix} \cos \frac{\theta}{2} & \sin \frac{\theta}{2} \\ -\sin \frac{\theta}{2} & \cos \frac{\theta}{2} \end{bmatrix}$$

around axis  $z$

$$R_z(\phi) = \begin{bmatrix} e^{i\frac{\phi}{2}} & 0 \\ 0 & e^{-i\frac{\phi}{2}} \end{bmatrix}$$

# Useful Unitary Gates

- Conditional Phase Shift

$$P(\varepsilon)|c_0 c_1 \dots c_{n-1}\rangle \rightarrow \begin{cases} e^{i\varepsilon}|c_0 c_1 \dots c_{n-1}\rangle, & \text{if } c_0 c_1 \dots c_{n-1} = 11 \dots 1 \\ |c_0 c_1 \dots c_{n-1}\rangle, & \text{otherwise} \end{cases}$$

$$P_{n-qubit}(\varepsilon) = \begin{bmatrix} 1 & 0 & 0 & \cdots & 0 \\ 0 & 1 & 0 & & \\ 0 & 0 & 1 & & \\ \vdots & & & \ddots & \vdots \\ & & & 1 & 0 \\ 0 & & \cdots & 0 & e^{i\varepsilon} \end{bmatrix}$$

# Useful Unitary Gates

- Conditional NOT Gate

$CNOT_{(n+1)-qubit}: |x_0, x_1 \dots, x_{n-1}, z\rangle \rightarrow |x_0, x_1 \dots, x_{n-1}, (\Lambda_{i=0}^{n-1} x_i) \otimes z\rangle$

$$CNOT = \begin{bmatrix} 1 & 0 & \cdots & & 0 \\ 0 & 1 & & & \\ \vdots & & \ddots & & \vdots \\ & & & 1 & 0 & 0 \\ 0 & & \cdots & 0 & 0 & 1 \\ & & & 0 & 1 & 0 \end{bmatrix}$$



# Quantum Functions

- Pseudo-classic operator  $f$  over  $n$  input qubits and  $m$  output qubits:

$$F_{n,m} : |k\rangle \otimes |0\rangle = |k,0\rangle \rightarrow |k, f(k)\rangle = |k\rangle \otimes |f(k)\rangle$$

- Could be applied over a superposition:

$$F : \frac{1}{\sqrt{n}} \sum_{i=0}^{2^n-1} |i\rangle |0\rangle \rightarrow \frac{1}{\sqrt{n}} \sum_{i=0}^{2^n-1} |i\rangle |f(i)\rangle$$

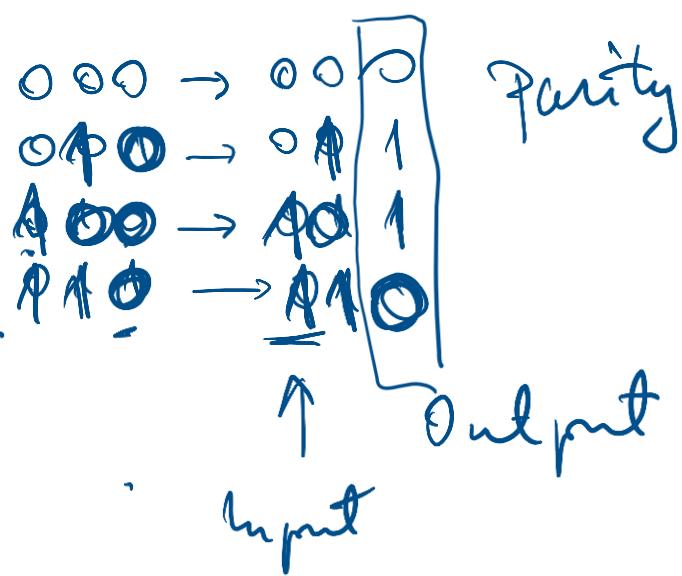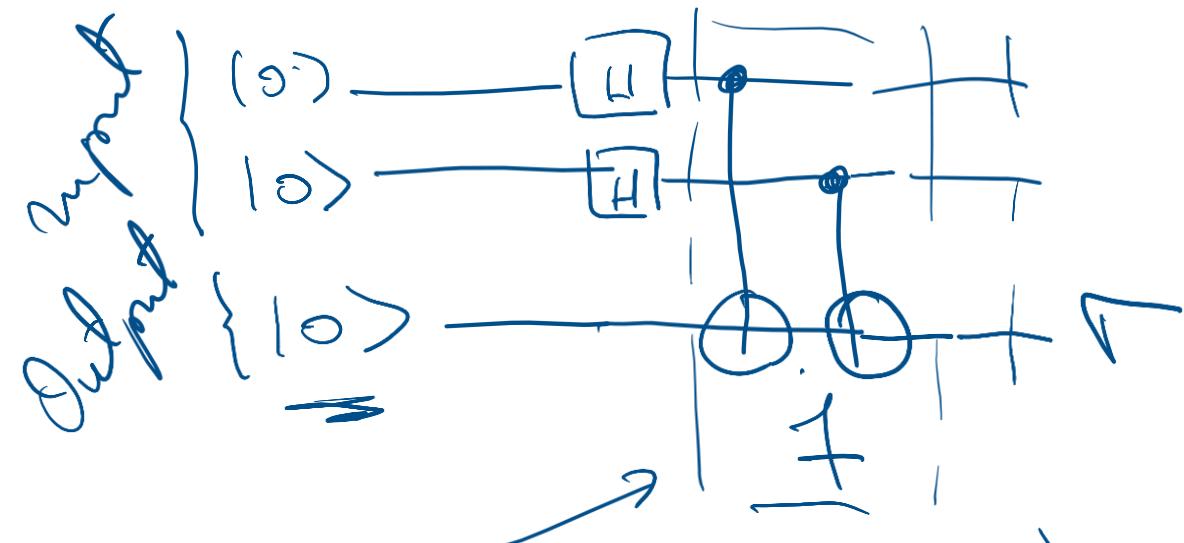

$$\frac{1}{2}(|000\rangle + |010\rangle + |100\rangle + |110\rangle) =$$

$$= \frac{1}{2}(|00\rangle + |01\rangle + |10\rangle + |11\rangle) \otimes |0\rangle$$

input register

$$\frac{1}{2}(|000\rangle + |011\rangle + |101\rangle + |110\rangle)$$

↓

output register

$$|q_1 q_2 q_3\rangle \xrightarrow{\text{input}} |q_1 q_2\rangle \otimes |q_3\rangle \xrightarrow{\text{output}}$$

$$\frac{1}{2}(|000\rangle + |011\rangle + |101\rangle + |110\rangle) \xrightarrow[\text{measurement}]{q_1 q_2 \rightarrow 01} |011\rangle$$

$$\frac{1}{2}(|000\rangle + \underline{|011\rangle} + \underline{|101\rangle} + |110\rangle) \xrightarrow[\text{measurement}]{q_3 \rightarrow 1}$$

$$\longrightarrow \frac{1}{\sqrt{2}}(|011\rangle + |101\rangle)$$

# Quantum Functions



- Measurement


$$\frac{1}{\sqrt{\frac{n}{2}}} \sum_{i=0}^{2^n-1} |i\rangle |f(i)\rangle \xrightarrow{\text{measurement}} |q\rangle |f(q)\rangle$$

- $f(j_0) = f(j_1) = \dots f(j_{w-1}) = q$


$$\frac{1}{\sqrt{\frac{n}{2}}} \sum_{i=0}^{2^n-1} |i\rangle |f(i)\rangle \xrightarrow{\text{measurement}} \frac{1}{\sqrt{w}} \sum_{i=0}^{w-1} |q\rangle |f(j_i)\rangle.$$

# Quantum adders

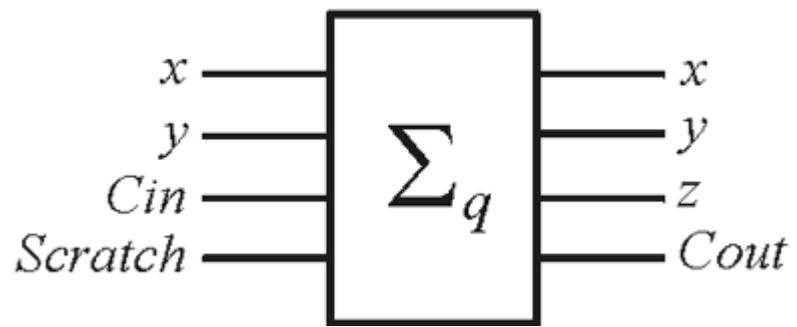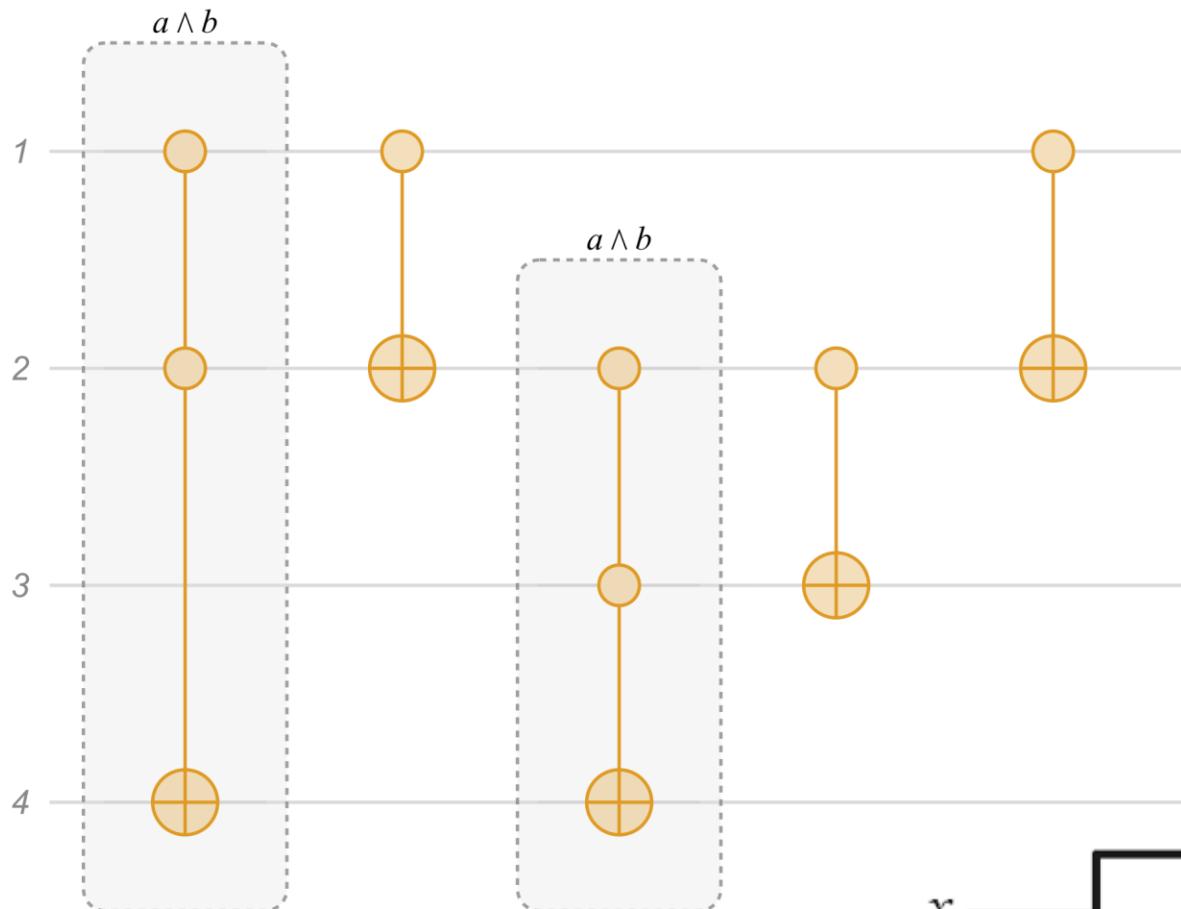

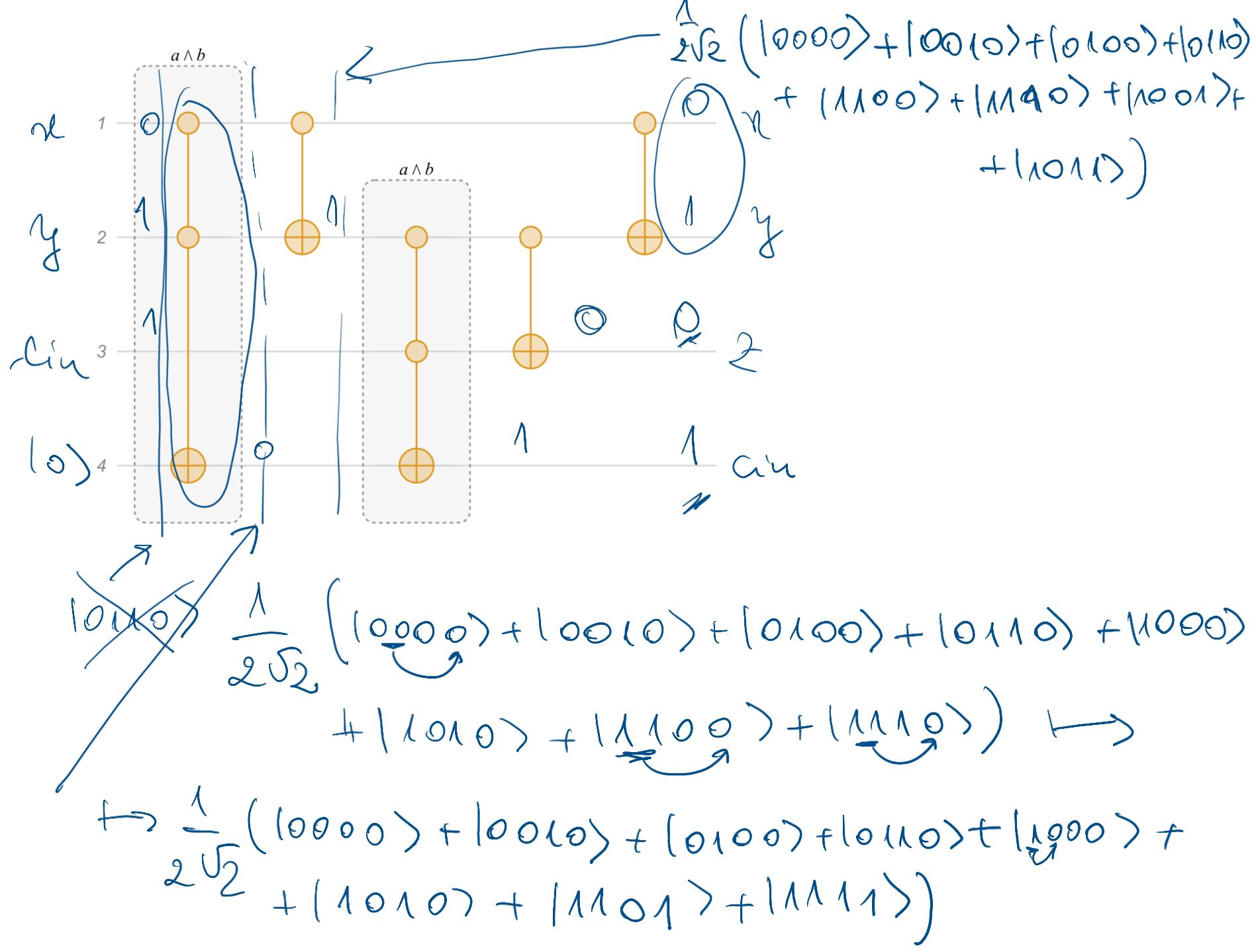


$$|1,2,3\rangle = |1101\rangle$$

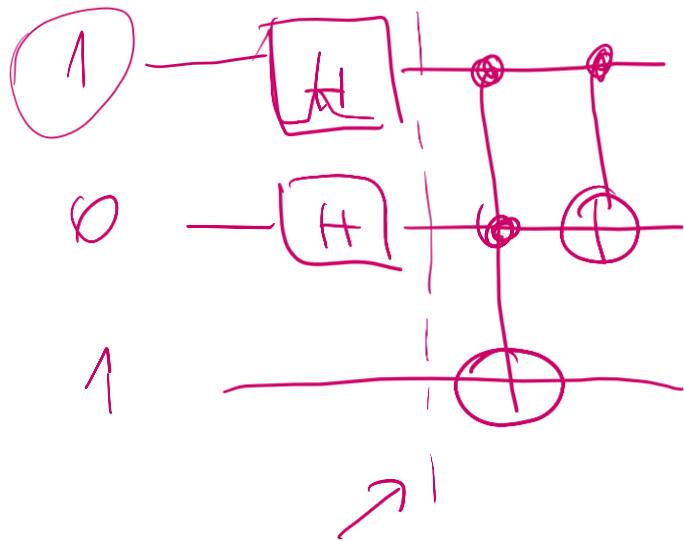

$$\begin{aligned} & \xrightarrow{\frac{1}{2}(|001\rangle + |011\rangle - |101\rangle - |111\rangle)} \\ & \downarrow \\ & \xleftarrow{\frac{1}{2}(|001\rangle + |011\rangle - |1101\rangle - |110\rangle)} \\ & \boxed{\frac{1}{2}(|001\rangle + |011\rangle - |111\rangle - |110\rangle)} \end{aligned}$$

$$\frac{1}{\sqrt{2}}(|0\rangle - |1\rangle) \otimes \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \otimes |1\rangle = \frac{1}{\sqrt{2}} \begin{pmatrix} 1 \\ 1 \\ -1 \end{pmatrix} \otimes \frac{1}{\sqrt{2}} \begin{pmatrix} 1 \\ 1 \\ 1 \end{pmatrix} \otimes$$

$$= \frac{1}{2} \begin{pmatrix} 1 \\ 1 \\ -1 \\ -1 \end{pmatrix} \otimes \begin{pmatrix} 0 \\ 1 \\ 0 \\ 1 \\ 0 \\ -1 \\ 0 \\ -1 \end{pmatrix} = \frac{1}{2} \begin{pmatrix} 0 \\ 1 \\ 0 \\ 1 \\ 0 \\ -1 \\ 0 \\ -1 \end{pmatrix} = \begin{pmatrix} 0 \\ 1 \\ 0 \\ 1 \\ 0 \\ -1 \\ 0 \\ -1 \end{pmatrix} = \begin{pmatrix} 1 \\ 1 \\ 0 \\ 0 \end{pmatrix} = \begin{pmatrix} 1 \\ 1 \\ 0 \\ 0 \end{pmatrix} \otimes \begin{pmatrix} 1 \\ 1 \\ 0 \\ 0 \end{pmatrix}$$



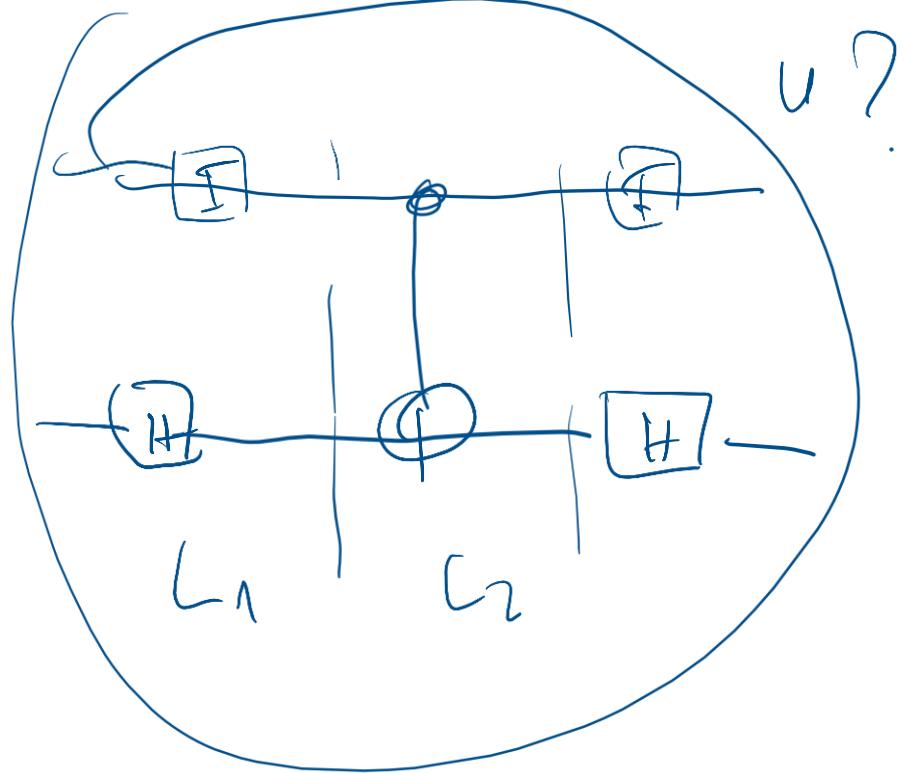


u?

$$(I \otimes H) \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{pmatrix} (I \otimes H)$$

$$I \otimes H = \begin{pmatrix} 1 & 0 \\ 0 & 1 \end{pmatrix} \otimes \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 \\ 1 & -1 \end{pmatrix} =$$

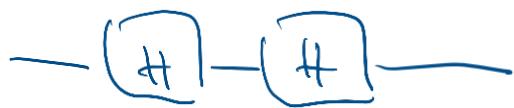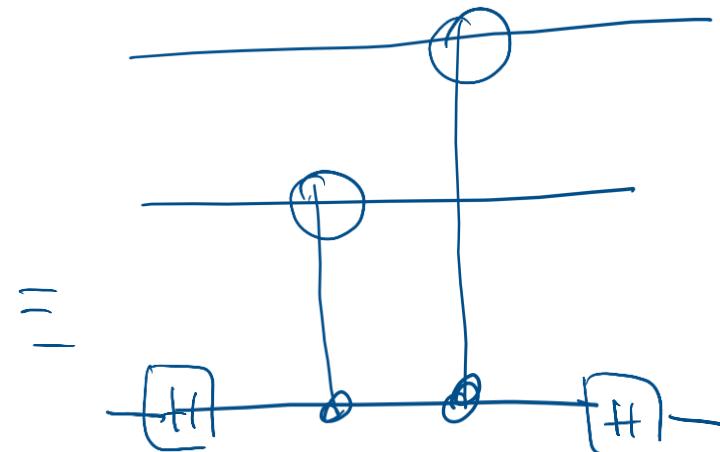
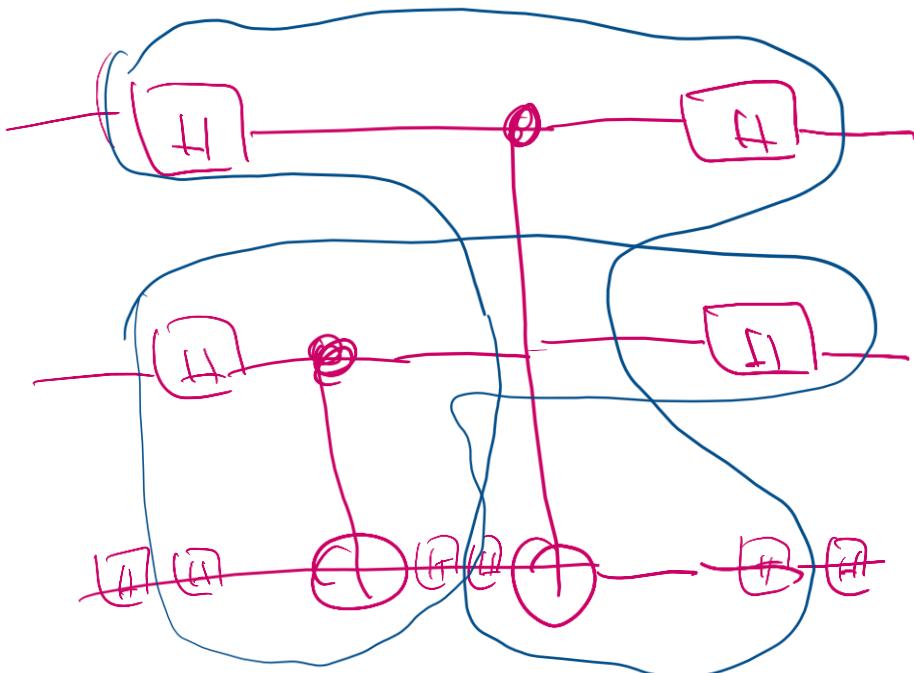
$$= \frac{1}{\sqrt{2}} \begin{pmatrix} 1 & 1 & 0 & 0 \\ 1 & -1 & 0 & 0 \\ 0 & 0 & 1 & 1 \\ 0 & 0 & 1 & -1 \end{pmatrix}$$



=




# Quantum adders

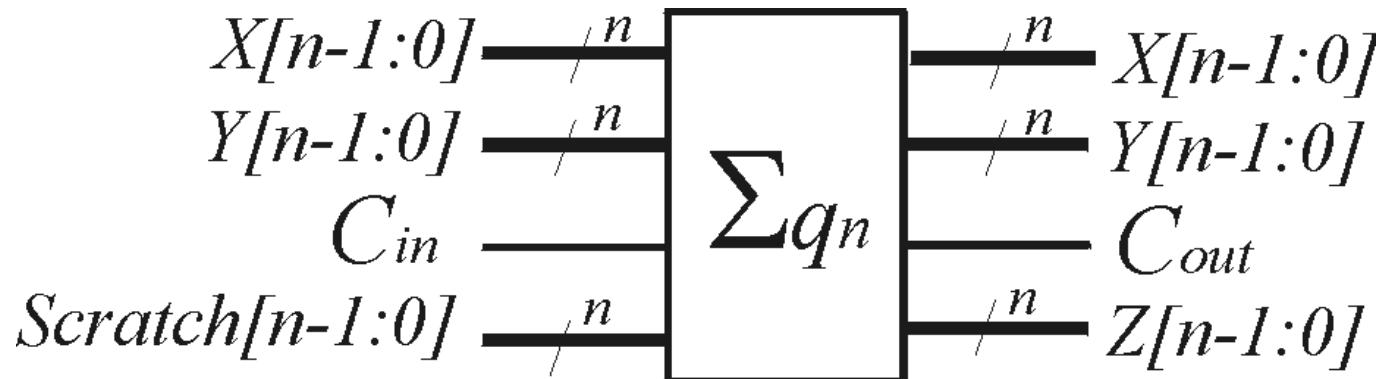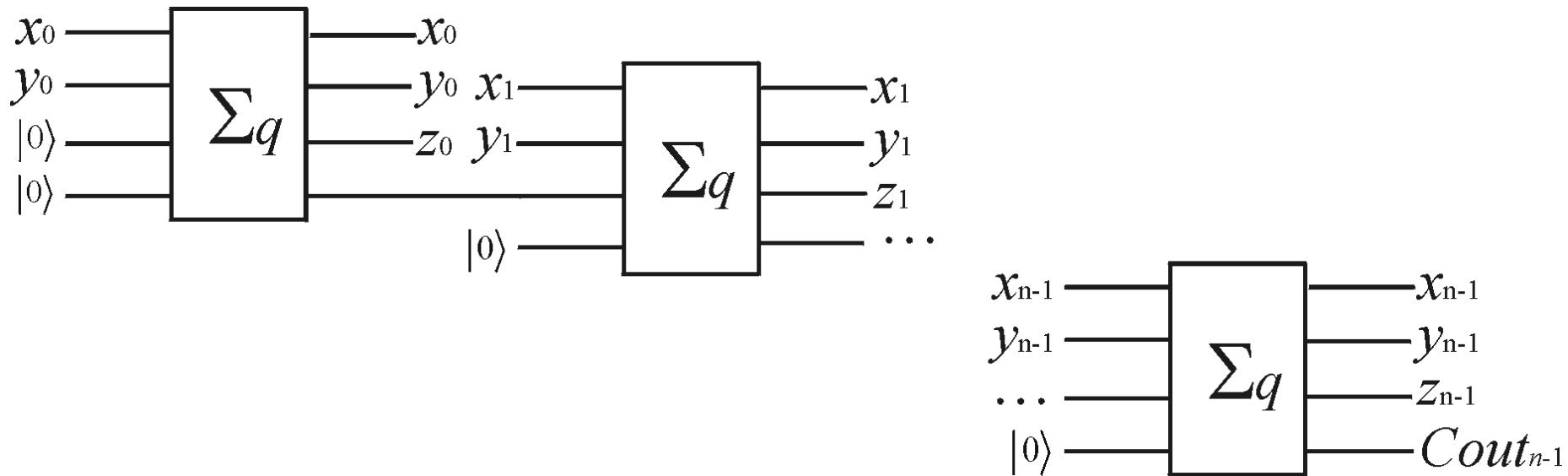


# Quantum adders


- Space saving

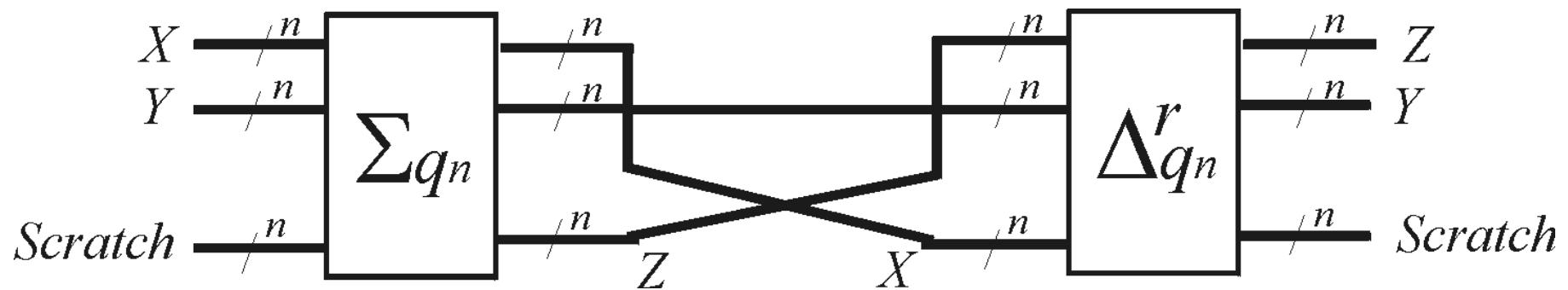


# Subtracting devices

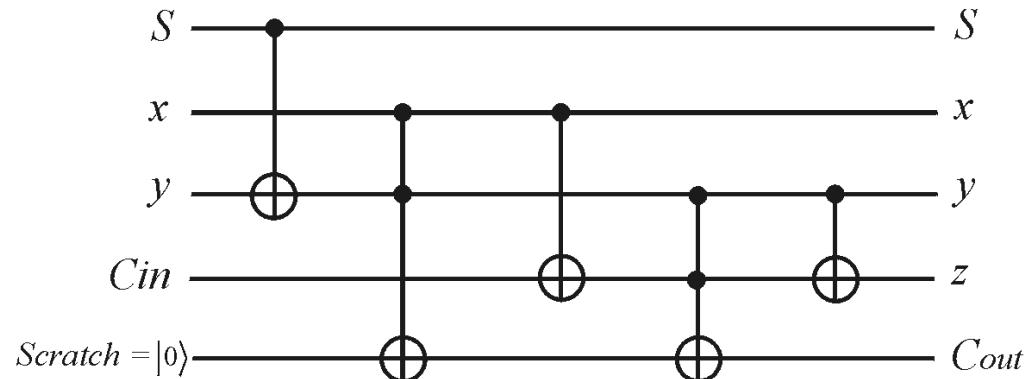

a)

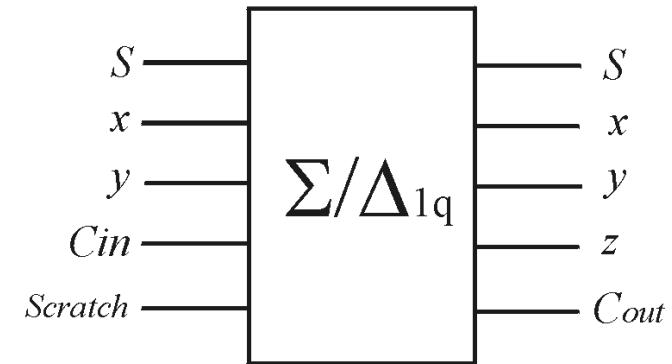

b)

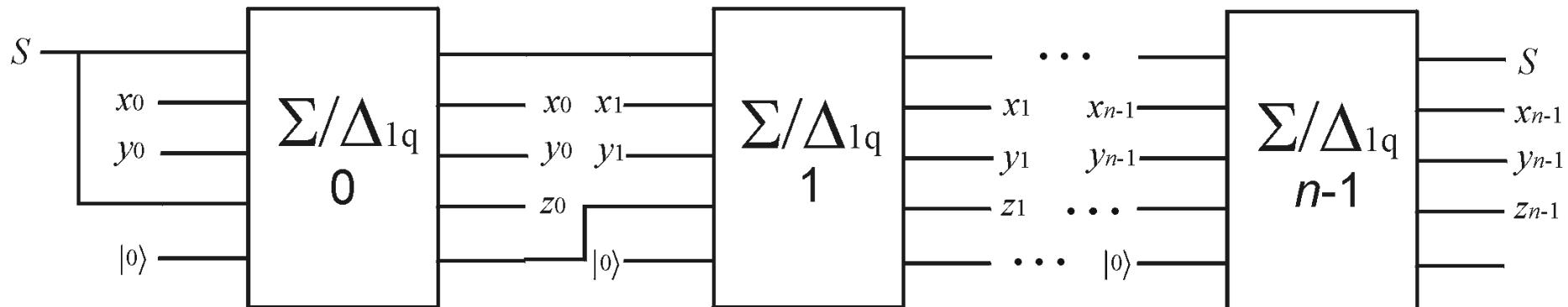

c)

# Unitary Synthesis

- Gate Family

$$\wedge_n(U) = \begin{pmatrix} 1 & & & & \\ & 1 & & & \\ & & \ddots & & \\ & & & 1 & \\ & & & & u_{00} \quad u_{01} \\ & & & & u_{10} \quad u_{11} \end{pmatrix}$$

- Universal Set in QC


$$\{\wedge_1(\sigma_x), \wedge_0(U)\}$$

# Unitary Level Design


- $\wedge_n(U)$  circuits




$\wedge_0(U)$

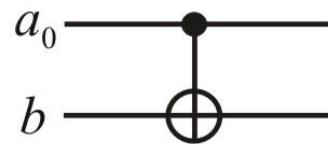

$\wedge_1(\sigma_x)$

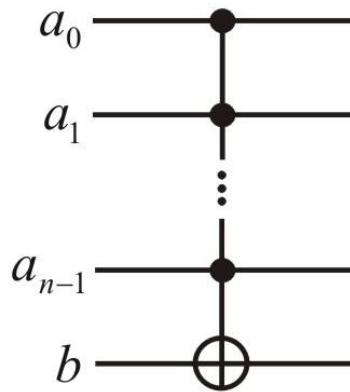

$\wedge_n(\sigma_x)$

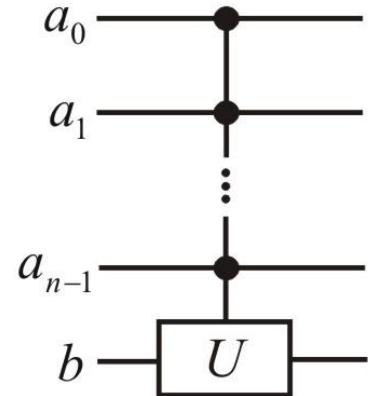

$\wedge_n(U)$

# Unitary Level Design


- Pauli Matrices

$$\sigma_x = \begin{pmatrix} 0 & 1 \\ 1 & 0 \end{pmatrix} \quad \sigma_y = \begin{pmatrix} 0 & -i \\ i & 0 \end{pmatrix}$$


$$\sigma_z = \begin{pmatrix} 1 & 0 \\ 0 & -1 \end{pmatrix}$$
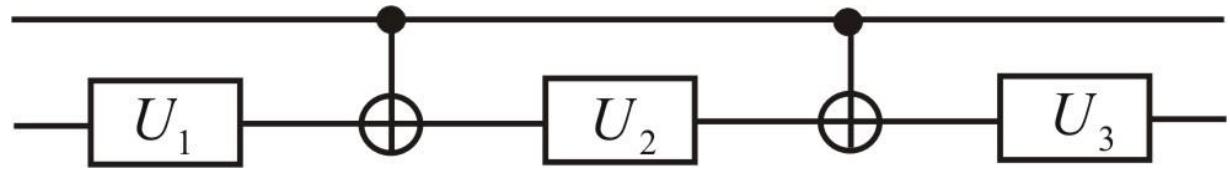
# Unitary Synthesis Rules

$$\wedge_1(U)$$
$$U = U_1 \cdot U_2 \cdot U_3$$




$$\wedge_2(U)$$
$$U = W^2$$

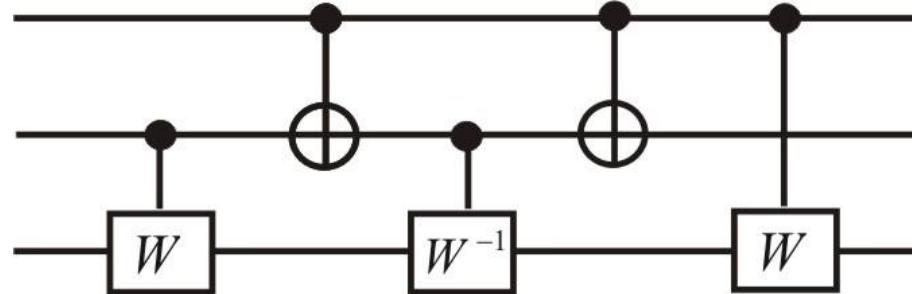

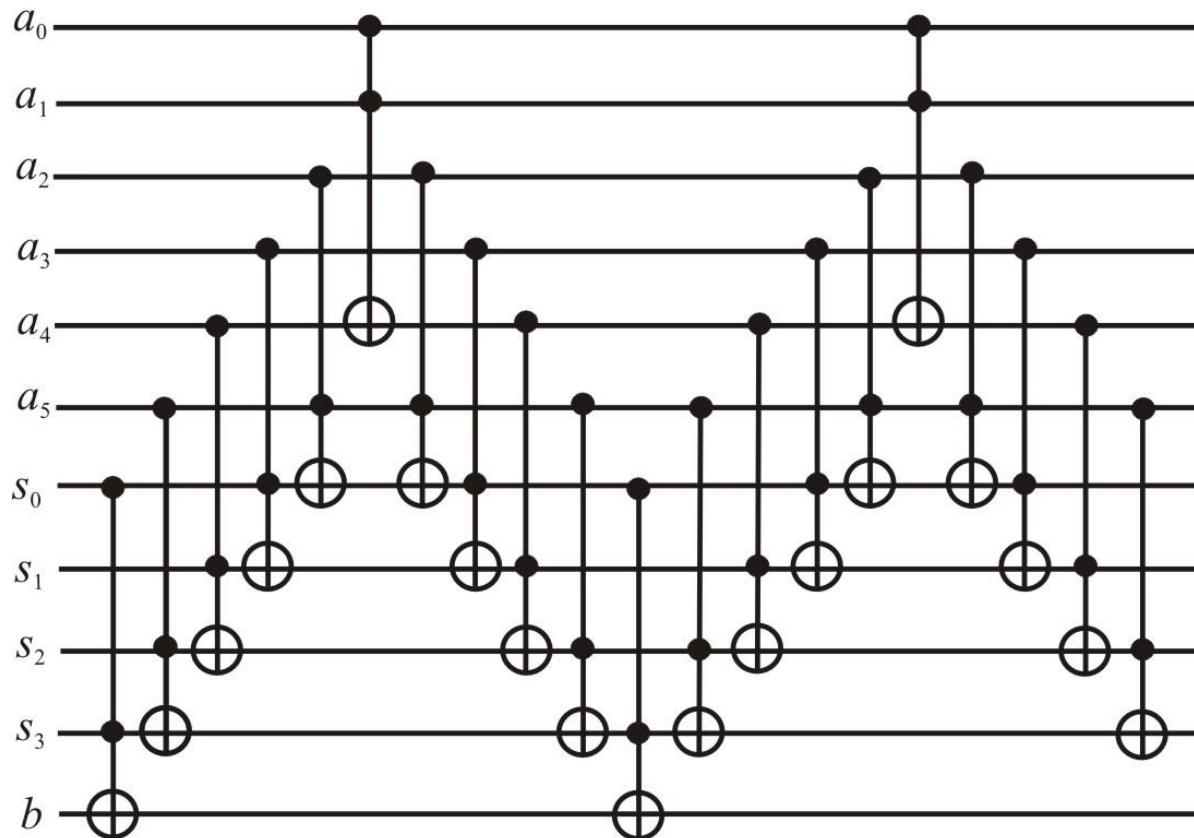
# Unitary Synthesis Rules

$\wedge_n(\sigma_x)$  from  $4(n-2) \times \wedge_2(\sigma_x)$  and  $(n-2) \times \text{scratch}$





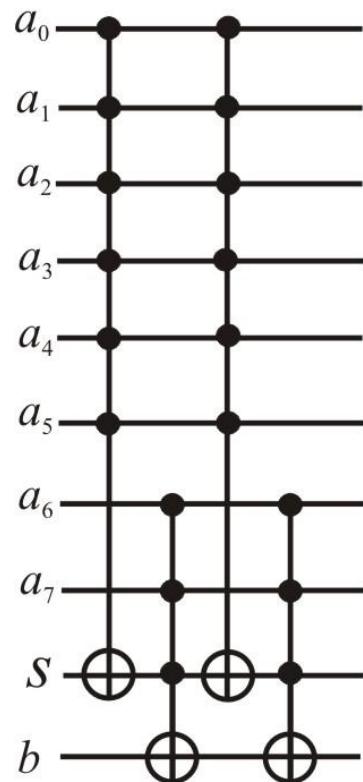
# Unitary Synthesis Rules

$\wedge_n(\sigma_x)$  from  $2 \times \wedge_m(\sigma_x)$  and  $2 \times \wedge_{n-m+1}(\sigma_x)$



# Unitary Synthesis Rules


$\wedge_n(U)$

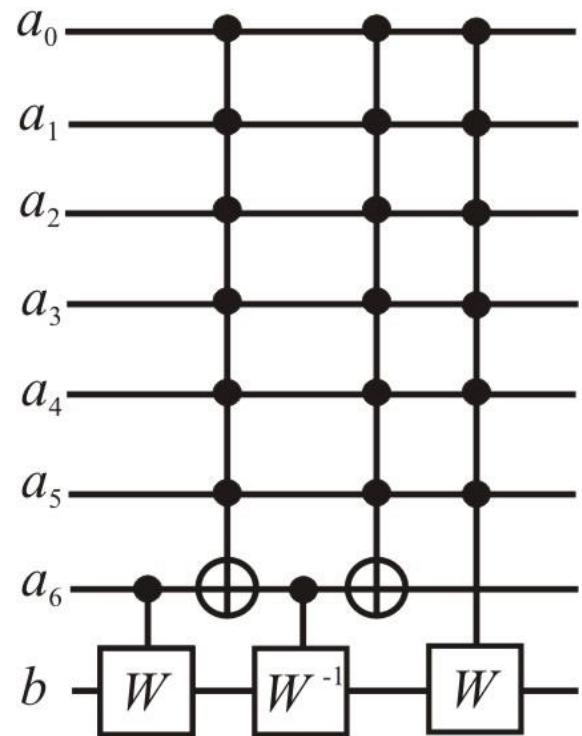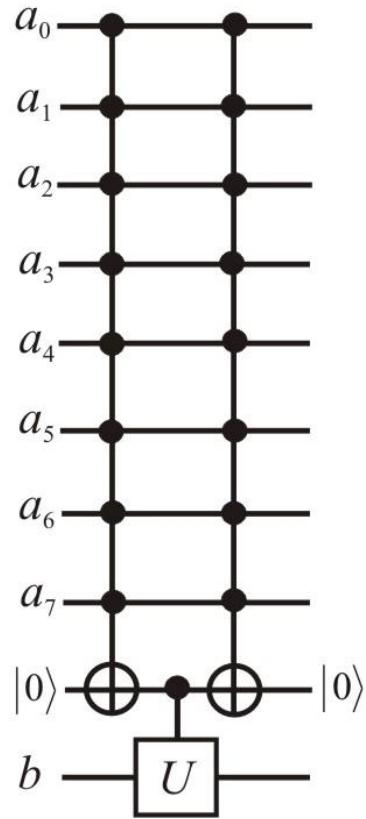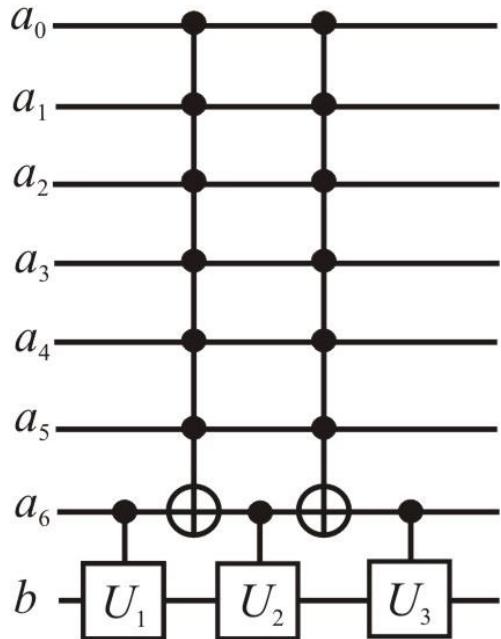


# Unitary Synthesis Refinements

- Qubit permutation

With scratch

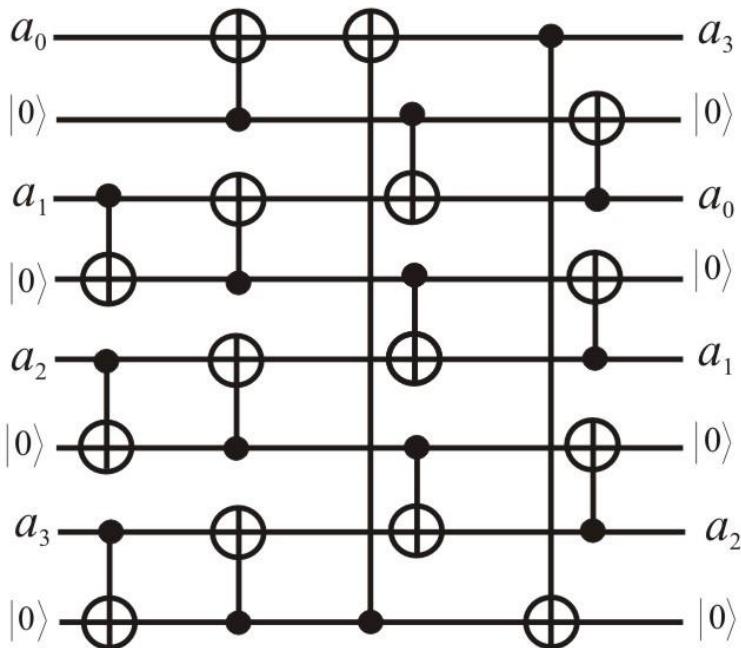


No scratch

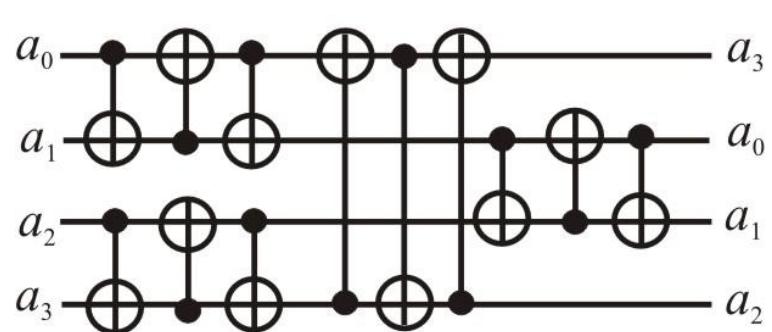
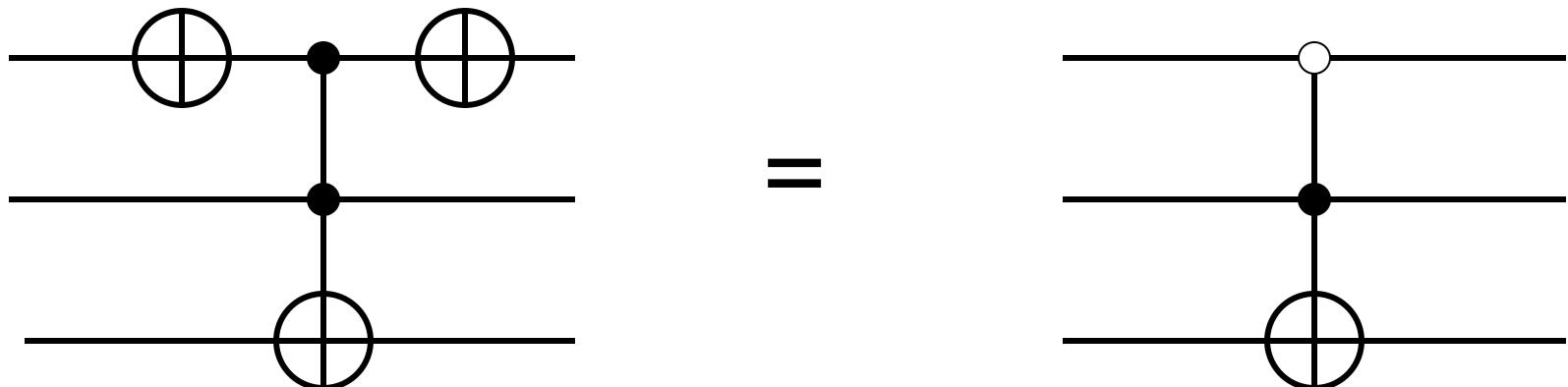
# Other Gates


Symmetric phase shift

$$\begin{array}{c} \text{Circuit Diagram: Two horizontal lines with a vertical control line connecting them. A dot labeled } \varepsilon \text{ is at the top junction.} \\ \wedge_1 \begin{pmatrix} 1 & 0 \\ 0 & e^{i\varepsilon} \end{pmatrix} \quad \varepsilon = \pi \Rightarrow \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & -1 \end{bmatrix} \end{array}$$




# Other Gates

Arbitrary diagonal gate

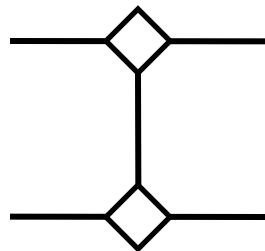

$$\begin{bmatrix} e^{i\xi_0} & 0 & 0 & 0 \\ 0 & e^{i\xi_1} & 0 & 0 \\ 0 & 0 & e^{i\xi_2} & 0 \\ 0 & 0 & 0 & e^{i\xi_3} \end{bmatrix}$$


Wiggle gate

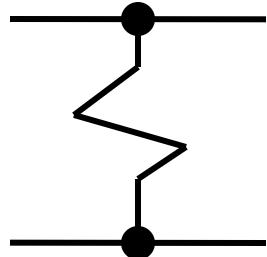


$$\frac{1}{2} \begin{bmatrix} 1 & 1 & 1 & -1 \\ 1 & 1 & -1 & 1 \\ 1 & -1 & 1 & 1 \\ -1 & 1 & 1 & 1 \end{bmatrix}$$

# Other Gates

Simpler notation

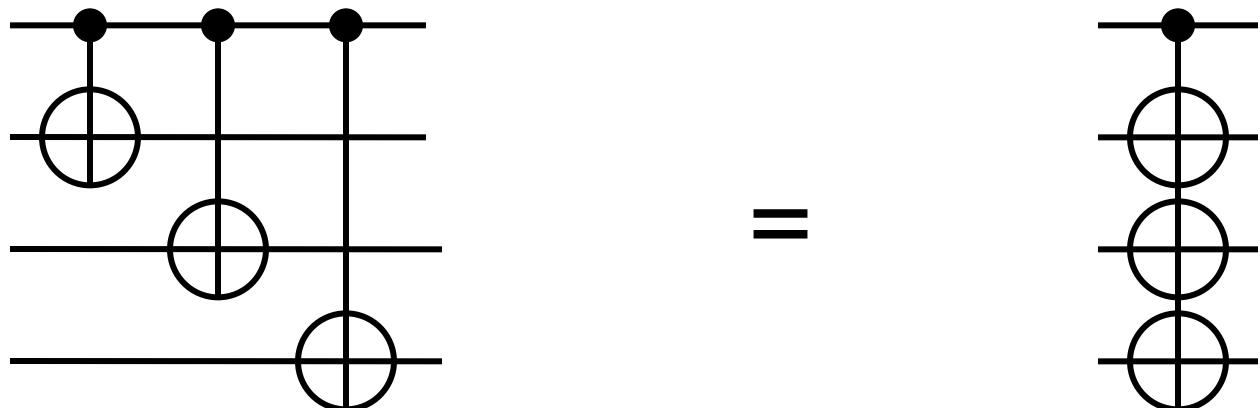


Multiple-qubit U

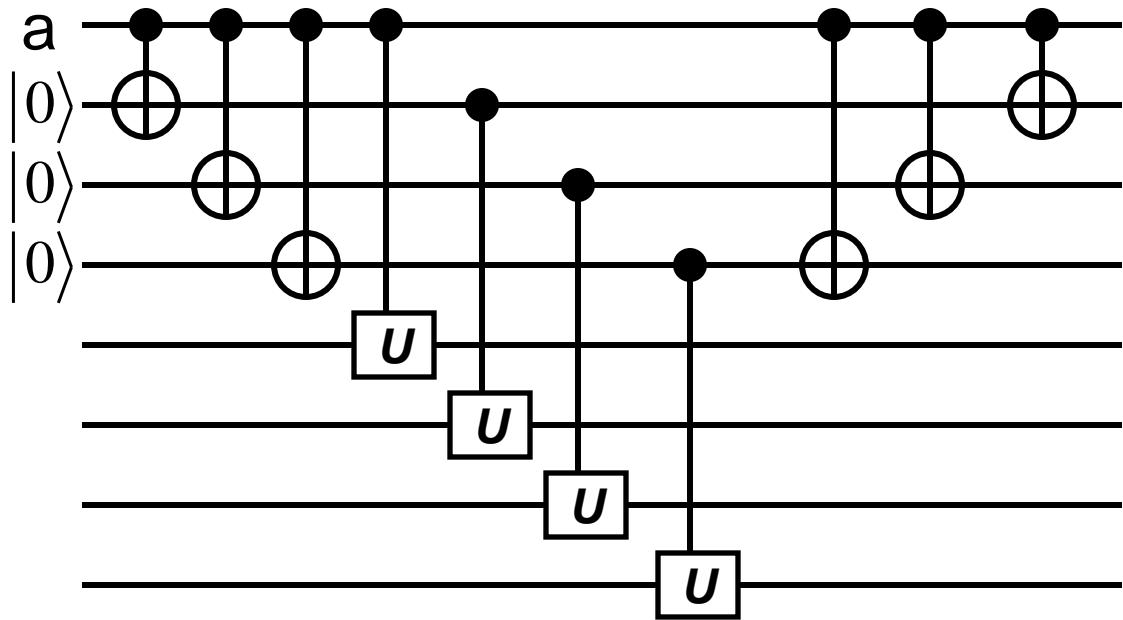



# Unitary Synthesis Refinements

- Parallelization

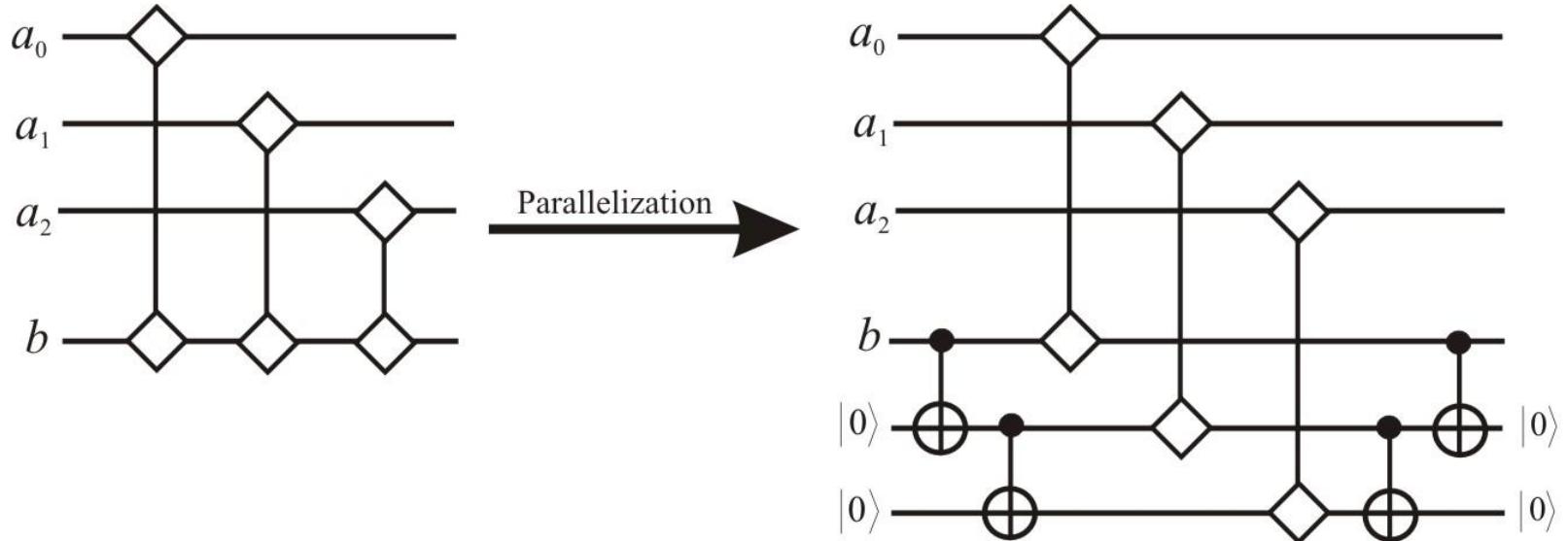



# Unitary Synthesis Refinements

- Quantum circuit coding

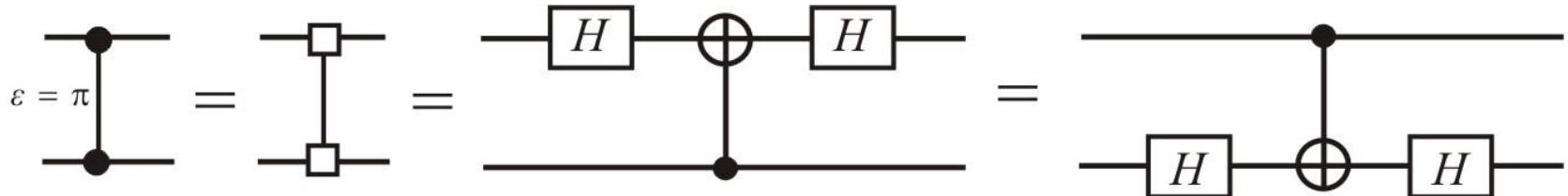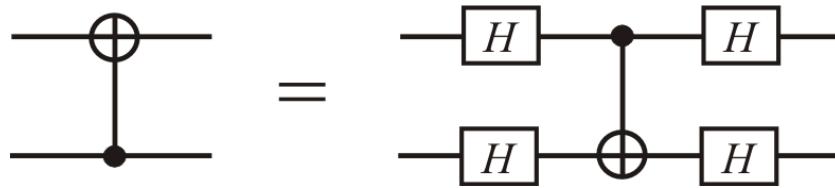



# Unitary Synthesis Refinements

- Quantum circuit coding

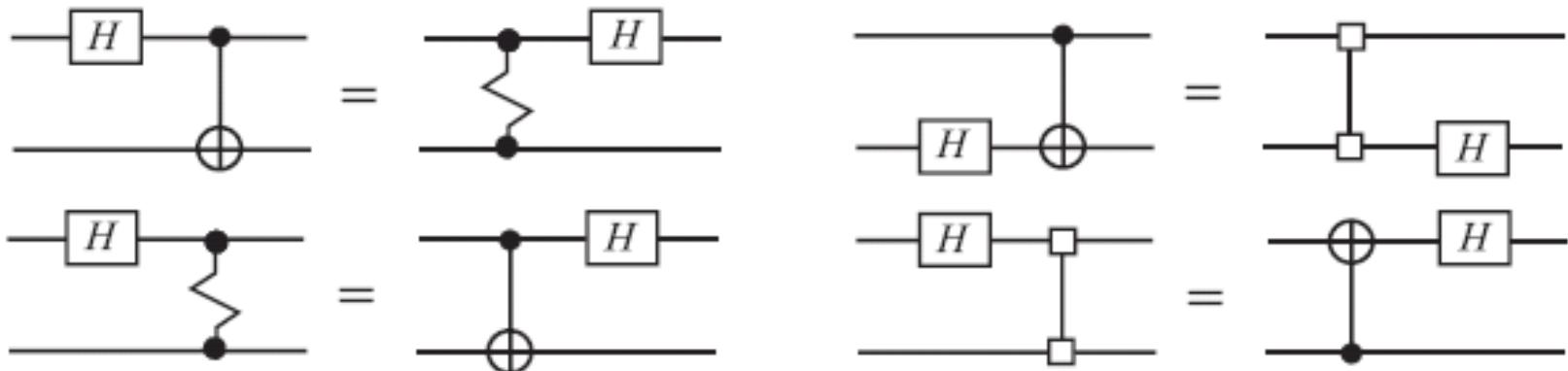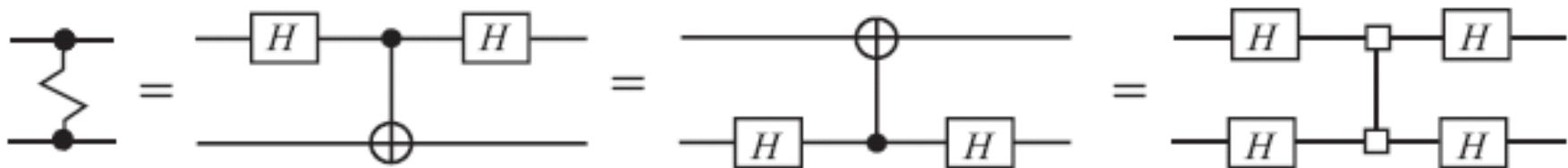

# Unitary Synthesis Refinements

- Example:  $\text{MOD}_2^4$

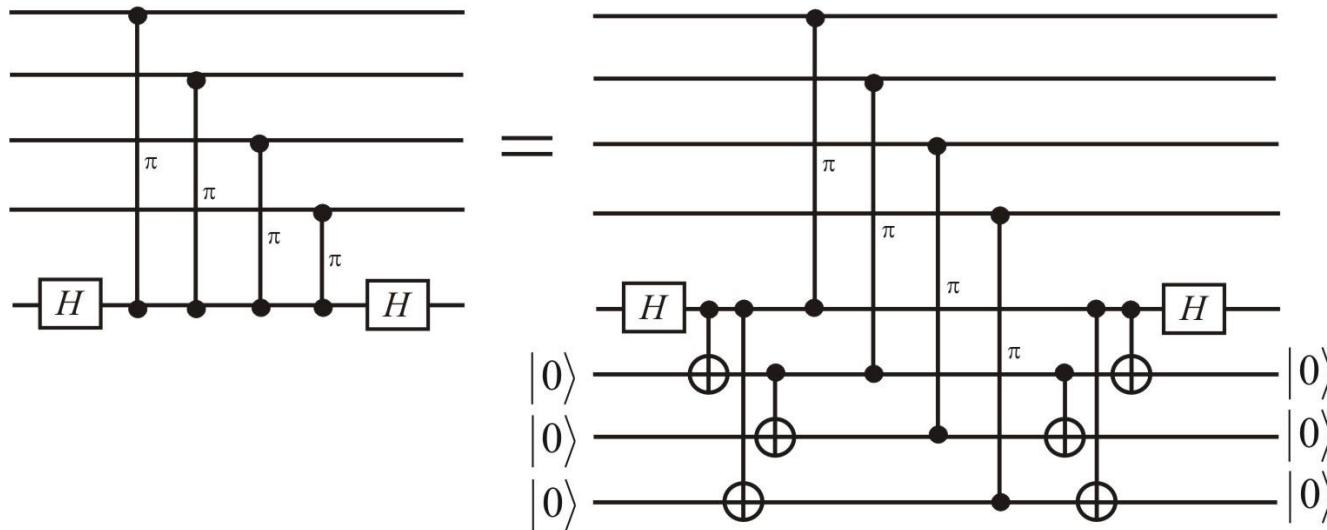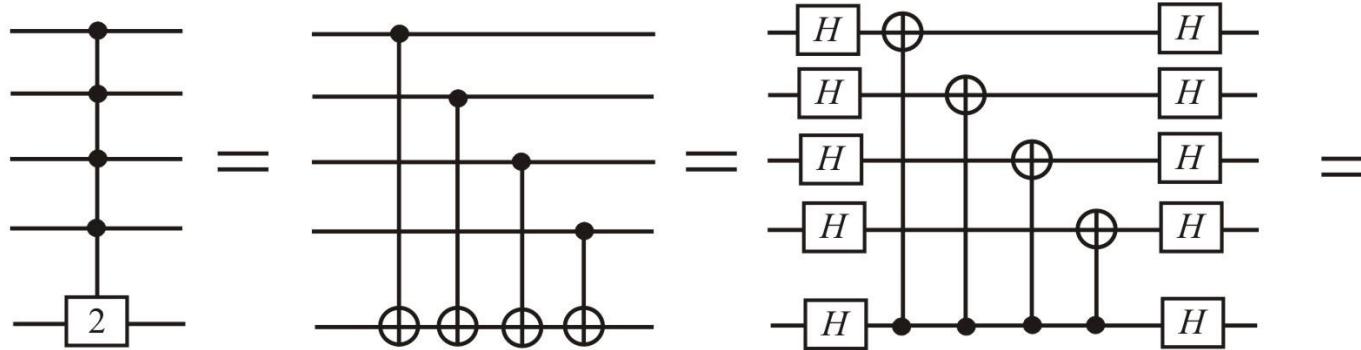

# Unitary Synthesis Refinements

- Example: Coppersmith's staircase circuit

